

Use an SCR or Triac in this Speed Control for Electric Drills

This simple SCR circuit allows "universal" or AC/DC brush-type motors to be used over a wide range of speeds while still maintaining good torque. While primarily intended for electric drills, it may also be used to control the speed of electric saws, food mixers and movie projectors.

by LEO SIMPSON

An electric hand drill is nowadays regarded as essential in any home handyman's tool kit, and with most handymen the drill is called upon to perform a multiplicity of jobs. Apart from the mundane jobs of drilling holes and powering various attachments such as circular saws and orbital sanders, it may also be called upon to stir paint and polish the family car. As versatile as the modern drill is, however, the chuck speed is often not low enough, even on the two speed models. This is a problem when larger drills and bits are used, particularly in the case of masonry drills.

Since the power source is the AC mains supply, the only convenient method of regulating the power fed to the drill motor is to use a thyristor device, either a silicon controlled rectifier (SCR) or a Triac.

The SCR device conducts in one direction only and thus feeds half-wave rectified AC to the motor. It operates in the following way. Basically an SCR behaves like a special sort of rectifier diode which only conducts in the forward direction if it is triggered into so doing by a small positive voltage applied between gate and cathode. When the anode to cathode current drops to zero or the anode-cathode voltage reverses, the device turns off, whereupon it must be triggered into conduction again when required by a

further application of voltage between gate and cathode.

An SCR is used to control the AC power fed to the load by varying the instant during each positive half-cycle (ie, when the anode-cathode voltage is positive) at which it is triggered into conduction. If the SCR is triggered early in each positive half-cycle, considerable power will be delivered to the load. On the other hand, if it is triggered late in each positive half-cycle, very little power is delivered to the load. This method of control is referred to as "phase control" since the phase of the SCR trigger point is varied with respect to the phase of the AC supply voltage.

The same method of control can be used with Triacs, except that Triacs conduct in both directions and can be triggered by positive or negative voltages applied between gate and terminal-1, the latter being the Triac equivalent of the SCR cathode.

The most economical circuit for motor speed control is very similar to that for a light dimmer using a Triac and diac. Such a circuit was published in the December 1969 issue of "Electronics Australia". This type of circuit will allow motor operation over a wide range of speeds but is really only suitable for motors that run at a constant load such as fans on furnaces and air-

conditioners. If the load on the motor varies, as is the case with electric drills and similar appliances, some means of sensing the speed is necessary so that the circuit can adjust to a changing load condition.

Unless a separate tachometer is used to measure the actual speed of the motor shaft, the only convenient way of monitoring the motor speed is to measure the back-EMF of the motor. (Back EMF is defined as a voltage developed by a motor which opposes the supply voltage.) The back EMF of any motor is basically a function of the speed but there is a problem with the motors used in hand drills and food mixers.

These are so-called universal motors — AC/DC series motors with commutators. The instant during each half cycle at which the SCR is triggered should be controlled by the back-EMF, but at the time the back-EMF is monitored, the SCR is not conducting and thus the field of a series motor is not excited. This means that with this type of motor, the actual back EMF monitored by the circuit will depend on the remanent magnetism of the motor and this will be a function of the current drawn in preceding half cycles.

In this respect, series AC/DC motors are not as convenient as shunt wound or permanent magnet motors which have an essentially constant field strength and hence a back EMF which is related to speed.


In the circuit, the motor is supplied with half-wave rectified AC via an SCR. As we shall see, this allows the motor back-EMF to be easily monitored and a wide range of operating speed to be achieved — wider in fact, than if full wave control was used.

The SCR used in the circuit can be one of three types that are readily available through parts suppliers: the C122D made by General Electric, the BT101/500R made by Philips and the 2SF28 made by ITT. These SCRs have a current rating of around 6 amps rms and a breakover voltage of 400V or more. For triggering, they require a positive voltage between gate and cathode of approximately 1 volt. Other SCRs with similar ratings may also be used.

As can be seen from the circuit, the SCR is connected in series with the output socket so that when the SCR is non-conducting, no power is supplied to the motor. A resistor chain consisting of a 10K and 1.8K resistor and a 2K potentiometer provide a positive-going reference voltage for the SCR gate, via diode D2. Diode D1 reduces the power dissipation in the resistor chain by half and protects the SCR gate when the supply voltage reverses and the load is open-circuit, as, for example, when the motor is switched off. Diode D2 isolates the trigger circuit when the SCR is in the conducting state.

The triggering voltage for the SCR is controlled by the setting of the 2K potentiometer. During each positive half-cycle of the AC supply (when D1 conducts) the pot provides a sinusoidal triggering voltage with amplitude variable from 20V to 50V RMS approximately. This is applied to the SCR gate via diode D2. The capacitor connected across the potentiometer should be ignored for the moment.

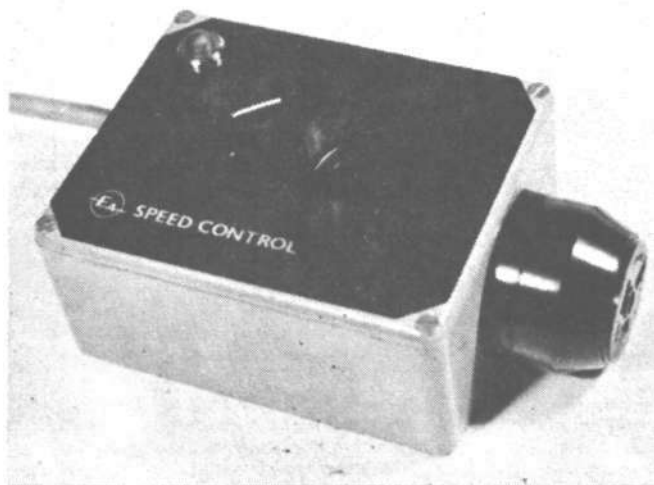The voltage supplied from the potentiometer is not the total effective SCR triggering voltage, because the motor is connected in series with the SCR cathode. This means that the SCR cathode is raised



The Speed Control was housed in a compact diecast aluminium box which is suitably robust.

As the motor back-EMF rises with increasing speed, the effective SCR triggering

the circuit would require a diode connected directly across the drill motor field winding, to ensure that the SCR would stop conducting at the end of each half-cycle. We felt that these additional complications were not worth the advantage of slightly higher available power.

Components to suppress radio interference have not been included in the circuit. Although the SCR switches on extremely rapidly, as does a Triac in a light dimmer circuit, the effective power being switched by the SCR is low. This is because the inductance in the motor stops any rapid rise in current, in contrast with what occurs with an incandescent lamp load in a light dimmer. In actual fact, the radio interference generated by an AC / DC brush type motor running from this type of SCR speed control circuit is less than if it is run directly from the mains. There is no reason why RF suppression capacitors should not be included, but for best effect they should be mounted in the motor housing itself.

The construction details of the speed control are quite simple, as may be seen from the photographs. While the approach we have used is not the only one possible, we do recommend that the unit be housed in a sturdy container, preferably a diecast box. The box we used measures 120 x 95 x 55mm and is available from most parts suppliers.

The SCR is mounted on a small heatsink measuring 60 x 40mm, made from 18-gauge aluminium. Since the case of the SCR is at mains potential, the plate must be isolated from the case by two insulating pillars. Take care that the SCR's threaded stud has at least 3mm clearance from the case.

As with many other SCR circuits, a Triac device may be substituted if its ratings are suitable. In fact the thyristor actually pictured in the photograph is a Triac. It has a current rating of 6 amps and is likely to be cheaper than the SCRs specified. In this circuit, a Triac will behave in exactly the same way as an SCR, triggering only on positive half-cycles. It will not give full-wave operation.

Most of the circuitry is mounted on a miniature 8-lug tagstrip, as shown by the wiring diagram. The 10K resistor is wired between a solder lug on the SCR heatsink and one of the tags on the strip. While we have used a 10 watt resistor, a 5 watt unit will be quite adequate. Note that none of the components in the circuit should make any physical contact with the metal case, which is earthed. An exception can be made in the case of the 10K resistor, if this is a ceramic-cased type. Here contact with the case will allow the resistor to run cooler.

The mains input cord should be passed through a grommetted hole in the case and securely anchored with a mains cord clamp. The earth wire is terminated on one of the lugs of the tagstrip which form the tagstrip feet. It is most important that you ensure to make a good earth connection to the case — for safety's sake. The output to the drill is via a standard 3-pin socket.

Note that with some SCRs having very low gate trigger voltages, the 1.8K resistor will be too high, so that the drill will run at a constant high speed, regardless of the setting of the speed control. The 1.8K resistor should be reduced to give a suitable minimum drill speed, with the potentiometer at minimum setting.

